

EE309 Project

RISC design Microprocessor

Shubham Birange, 160070014

Pravesh Trivedi, 160070041

Parshva Shah, 160070009

Bhuyashi Deka, 16D070015

November 28, 2018

1 Overview

The aim of this project was to implement a fully functional RISC based computer design, IITB RISC whose ISA is provided below. IITB RISC is a 8 - register, 16-bit architecture using multi-cycle implementation.

Instructions Encoding:

ADD:	00_00	RA	RB	RC	0	00
ADC:	00_00	RA	RB	RC	0	10
ADZ:	00_00	RA	RB	RC	0	01
ADI:	00_01	RA	RB	6 bit Immediate		
NDU:	00_10	RA	RB	RC	0	00
NDC:	00_10	RA	RB	RC	0	10
NDZ:	00_10	RA	RB	RC	0	01
LHI:	00_11	RA	9 bit Immediate			
LW:	01_00	RA	RB	6 bit Immediate		
SW:	01_01	RA	RB	6 bit Immediate		
LM:	01_10	RA	0 + 8 bits corresponding to Reg R7 to R0			
SM:	01_11	RA	0 + 8 bits corresponding to Reg R7 to R0			
BEQ:	11_00	RA	RB	6 bit Immediate		
JAL:	10_00	RA	9 bit Immediate offset			
JLR:	10_01	RA	RB	000_000		

RA: Register A

RB: Register B

RC: Register C

 


Figure 2: State Transition graph of the controller

3 Instructions

The following are the hardware flowcharts for the ISA:

3.1 Arithmetic and logical Instructions

ADD/ ADC/ ADZ/ NDU/ NDC/ NDZ

PC → Mem-a, ALU_a Mem-d → IR +1 → ALU_b ALU_out → PC	CURRENT STATE HKT
	NEXT STATE rf_read
IR 9-11 → rf_a1 IR 6-8 → rf_a2 rf_d1 → T1 rf_d2 → T2	rf_read
if (IR is ADC/NDC and !C) or (IR is ADZ/NDZ and !Z) then PC → R7	if IR is ADD/NDU then alu_op elseif IR is ADC/NDC then if C then alu_op else HKT elseif IR is ADZ/NDZ then if Z then alu_op else HKT else HKT
T1 → ALU_a T2 → ALU_b ALU_out → T1	alu_op
	rf_write
IR 3-5 → rf_a3 T1 → rf_d3 if rf_a3 == '7' then rf_d3 → PC else PC → r7_in	rf_write
	HKT

ADI

PC → Mem-a, ALU_a Mem-d → IR +1 → ALU_b ALU_out → PC	CURRENT STATE HKT
	NEXT STATE rf_read
IR 9-11 → rf_a1 IR 6-8 → rf_a2 rf_d1 → T1 rf_d2 → T2	rf_read
	if IR is ADD/NDU/ADI then alu_op elseif IR is ADC/NDC then if C then alu_op else HKT elseif IR is ADZ/NDZ then if Z then alu_op else HKT else HKT
T1 → ALU_a IR 0-5 → SE6 → ALU_b ALU_out → T1	alu_op
	rf_write
IR 3-5 → rf_a3 T1 → rf_d3 if rf_a3 == '7' then rf_d3 → PC else PC → r7_in	rf_write
	HKT

3.2 LOAD LW

LW

PC → Mem-a, ALU_a Mem-d → IR +1 → ALU_b ALU_out → PC	CURRENT STATE HKT
	NEXT STATE rf_read
IR 8-6 → rf_a1 XX → rf_a2 rf_d1 → T1 rf_d2 → T2	rf_read
	if IR is ADD/NDU/ADI then alu_op elseif IR is ADC/NDC then if C then alu_op else HKT elseif IR is ADZ/NDZ then if Z then alu_op else HKT elseif IR is LHI then rf_write elseif IR is LW then compute_add. else HKT
T1 → ALU_a IR 0-5 → SE6 → ALU_b ALU_out → T1	compute_add.
	LOAD

T1 → Mem-a Mem-d → T2	LOAD
	alu_op
'0' → ALU_a T2 → ALU_b ALU_out → T1	alu_op.
	rf_write
IR 9-11 → rf_a3 T1 → rf_d3 if rf_a3 == '7' then rf_d3 → PC else PC → r7_in	rf_write
	HKT

3.3 STORE SW and LOAD LHI

LHI

PC → Mem-a, ALU_a Mem-d → IR +1 → ALU_b ALU_out → PC	CURRENT STATE HKT
	NEXT STATE rf_read
IR 9-11 → rf_a1 IR 6-8 → rf_a2 rf_d1 → T1 rf_d2 → T2	rf_read
	if IR is ADD/NDU/ADI then alu_op elseif IR is ADC/NDC then if C then alu_op else HKT elseif IR is ADZ/NDZ then if Z then alu_op else HKT elseif IR is LHI then rf_write else HKT
IR 11-9 → rf_a3 IR 8-0 → rf_d3 if rf_a3 == '7' then rf_d3 → PC else PC → r7_in	rf_write
	HKT

SW

PC → Mem-a, ALU_a Mem-d → IR +1 → ALU_b ALU_out → PC	CURRENT STATE HKT
	NEXT STATE rf_read
IR 8-6 → rf_a1 IR 9-11 → rf_a2 rf_d1 → T1 rf_d2 → T2	rf_read
	if IR is ADD/NDU/ADI then alu_op elseif IR is ADC/NDC then if C then alu_op else HKT elseif IR is ADZ/NDZ then if Z then alu_op else HKT elseif IR is LHI then rf_write elseif IR is LW/SW then compute_add. else HKT
T1 → ALU_a IR 0-5 → SE6 → ALU_b ALU_out → T1	compute_add.
	if IR is LW then LOAD elseif IR is SW then STORE
T1 → Mem-a T2 → Mem-d PC → r7_in	STORE
	HKT

3.4 LOAD Multiple LM

LM

PC → Mem-a, ALU_a Mem-d → IR +1 → ALU_b ALU_out → PC	CURRENT STATE HKT
	NEXT STATE rf_read
IR 11-9 → rf_a1 XX → rf_a2 rf_d1 → T1 If IR is LM then IR 0-7 → enco_register	rf_read
	if IR is ADD/NDU/ADI then alu_op elseif IR is ADC/NDC then if C then alu_op else HKT elseif IR is ADZ/NDZ then if Z then alu_op else HKT elseif IR is LHI then rf_write elseif IR is LW/SW then compute_add elseif IR is LM then LOAD_multi else HKT
T1 → Mem-a Mem-d → T2 T1 → ALU_a +1 → ALU_b ALU_out → T1	LOAD_multi
	LM_write

enco_address → rf_a3 T2 → rf_d3 if rf_a3 == '7' then rf_d3 → PC update enco_register by enoc_sel = '0' x <= Enco_register AND Decoder_o/p if X == '0' and IR(7) == '0' then PC → r7_in	LM_write if x is '1' then LOAD_multi else HKT
--	---

3.5 STORE Multiple SM

SM

PC → Mem-a, ALU_a Mem-d → IR +1 → ALU_b ALU_out → PC	CURRENT STATE HKT
	NEXT STATE rf_read
IR 11-9 → rf_a1 XX → rf_a2 rf_d1 → T1 If IR is LM/SM then IR 0-7 → enco_register	rf_read
	if IR is ADD/NDU/ADI then alu_op elseif IR is ADC/NDC then if C then alu_op else HKT elseif IR is ADZ/NDZ then if Z then alu_op else HKT elseif IR is LHI then rf_write elseif IR is LW/SW then compute_add elseif IR is LM then Load_multi elseif IR is SM then SM_read else HKT
Encoder Address → rf_a2 rf_d2 → T2	SM_read
	STORE_multi

T1 → Mem-a T2 → Mem-d T1 → ALU_a +1 → ALU_b ALU_out → T1 update enco_register by enoc_sel = '0' x <= Enco_register AND Decoder_o/p if X == '0' then PC → r7_in	STORE_multi if x is '1' then SM_read else HKT
---	--

3.6 Branch JAL and JLR

JAL

PC → Mem-a, ALU_a Mem-d → IR +1 → ALU_b ALU_out → PC		CURRENT STATE HKT
		NEXT STATE rf_read
'XX' → rf_a1 '7' → rf_a2 rf_d2 → T2 (PC → T2) if IR is LM/SM then IR 0-7 → enco_register		rf_read if IR is ADD/NDU/ADI then alu_op elseif IR is ADC/NDC then if C then alu_op else HKT elseif IR is ADZ/NDZ then if Z then alu_op else HKT elseif IR is LHI then rf_write elseif IR is LW/SW then compute_add . elseif IR is LM/SM then compare elseif IR is BEQ then BEQ_compare elseif IR is JAL then Jump else HKT
IR 8-0 → SE9 → ALU_a T2 → ALU_b ALU_out → PC IR 9-11 → rf_a3 T2 → rd_d3 if rf_a3 == '7' then rf_d3 → PC_in else PC_in → r7_in		JUMP
		HKT

JLR

PC → Mem-a, ALU_a Mem-d → IR +1 → ALU_b ALU_out → PC		CURRENT STATE HKT
		NEXT STATE rf_read
IR 8-6 → rf_a1 '7' → rf_a2 rf_d1 → T1 rf_d2 → T2 (PC → T2) if IR is LM/SM then IR 0-7 → enco_register		rf_read if IR is ADD/NDU/ADI then alu_op elseif IR is ADC/NDC then if C then alu_op else HKT elseif IR is ADZ/NDZ then if Z then alu_op else HKT elseif IR is LHI then rf_write elseif IR is LW/SW then compute_add . elseif IR is LM/SM then compare elseif IR is BEQ then BEQ_compare elseif IR is JAL then Jump elseif IR is JLR then JLR else HKT
T1 → PC IR 9-11 → rf_a3 T2 → rd_d3 if rf_a3 == '7' then rf_d3 → PC_in else PC_in → r7_in		JLR
		HKT

3.7 Branch BEQ

BEQ

PC → Mem-a, ALU_a Mem-d → IR +1 → ALU_b ALU_out → PC		CURRENT STATE HKT
		NEXT STATE rf_read
IR 11-9 → rf_a1 IR 8-6 → rf_a2 rf_d1 → T1 rf_d2 → T2 if IR is LM/SM then IR 0-7 → enco_register		rf_read if IR is ADD/NDU/ADI then alu_op elseif IR is ADC/NDC then if C then alu_op else HKT elseif IR is ADZ/NDZ then if Z then alu_op else HKT elseif IR is LHI then rf_write elseif IR is LW/SW then compute_add . elseif IR is LM/SM then compare elseif IR is BEQ then BEQ_compare else HKT
T1 → ALU_a T2 → ALU_b ALU_out → T1 (do not modify Z flag) if Z = '0' then PC_out → r7_in		BEQ_compare
		if Z then Load_PC else HKT

'7' → rf_a1 rf_d1 → T1		Load_PC
		Branch
T1 → ALU_a IR 0-5 → SE6 → ALU_b ALU_out → PC PC_in → r7_in		Branch
		HKT

4 Testing

The testing and verification of the design was done using the following code:

```
0 => "0001100100000111",--ADI R4 R4 111
1 => "0001101101000010",--ADI R5 R5 10
2 => "0111110000100000",--SM R6 00100000
3 => "0101100110000001",--SW R4 R6 01
4 => "0011100000000000",--LHI R4 0000
5 => "0011101000000000",--LHI R5 0000
6 => "0001011011000111",--ADI R3 R3 7
7 => "0110101000000110",--LM R5 00000110
8 => "1100001101000011",--BEQ R1 R5 3
9 => "0001001001111111",--ADI R1 R1 -1
10 => "1000110111111110",--JAL R6 -2
11 => "1100010101000100",--BEQ R2 R5 4
12=> "0001010010111111",--ADI R2 R2 -1
13=> "0100001101000001",--LW R1 R5 1
14=> "1000110111111010",--JAL R6 -6
15=> "0001000000000001",--ADI R0 R0 1
16=> "0011110000000000",--LHI R6 0
17=> "0001110110000011",--ADI R6 R6 3
18=> "1100000110000010",--BEQ R6 R0 +2
19=> "0000101011111000",--ADD R5 R3 R7
20=> "0011000000000000",--LHI R0 0
21=> "0000101011111000",--ADD R5 R3 R7
```

This is equivalent to:

```
R0 = 0
for(R1 = 7, R1 < 0, R1--)
  for(R2 j = 2, R2 < 0, R2--)
    if(R0 = 3)
      R0 = 0
    else
      R0++
```

4.1 Simulation Results

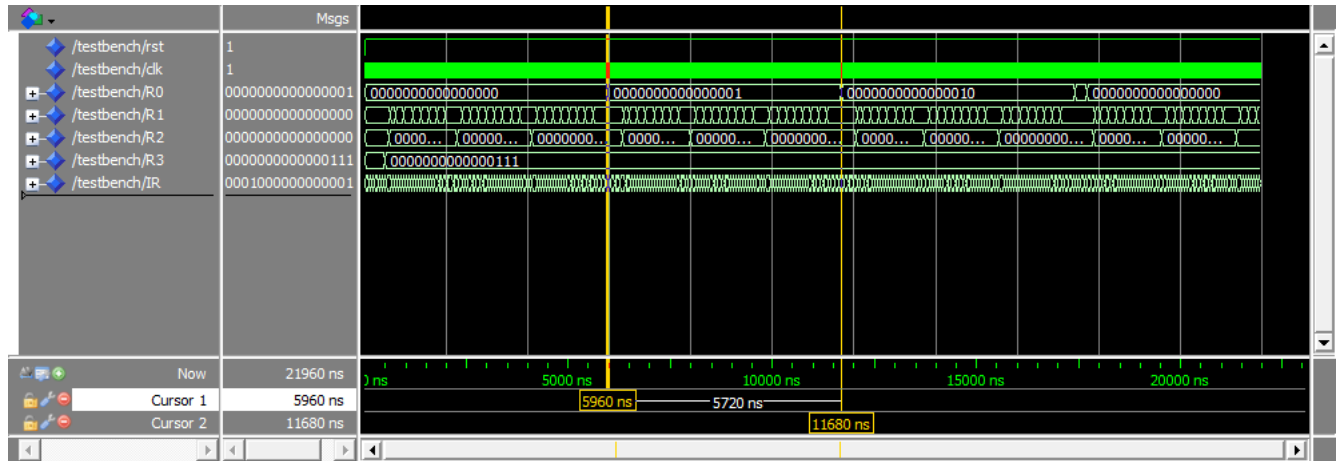


Figure 3: RTL simulation for the above code. Note the time for R0 to change is 5.72us

5 Code VHDL Files

1. **alu.vhd** - contains the code for the alu used in the design. It can perform addition, subtraction and nand operation on 16-bit numbers with the respective carry and zero flags.
2. **busmultiplexer.vhd** - code for a generic input 2^n multiplexer.
3. **controller.vhd** - contains the code for the FSM which decodes the instruction and gives the control signals as output.
4. **encoder.vhd** - contains the priority encoder and decoder used for decoding the address in LM and SM instructions.
5. **processor.vhd** - this is the top-level entity that combines all the components of the datapath and controller.
6. **RAM.vhd** - used as the RAM in the processor containing 16-bit data-in, data-out and an address bus.
7. **reg-file.vhd** - contains the code for the 8 registers and the multiplexers for selecting them.
8. **ROM.vhd** - memory containing the instructions.
9. **register.vhd** - generic n-bit register